



**Faculty of Engineering & Technology
Electrical & Computer Engineering Department**

CIRCUIT ANALYSIS ENEE2304

The Project

Prepared by:

Mohammad Abu Shams


1200549

Instructor: Dr. Hakam Shehadeh

Section: 2

Date: 15-6-2022

Question 1: Construct a PSPICE schematic for the circuit shown in the figure below. Simulate the schematic and show voltages at each node and current in each branch.

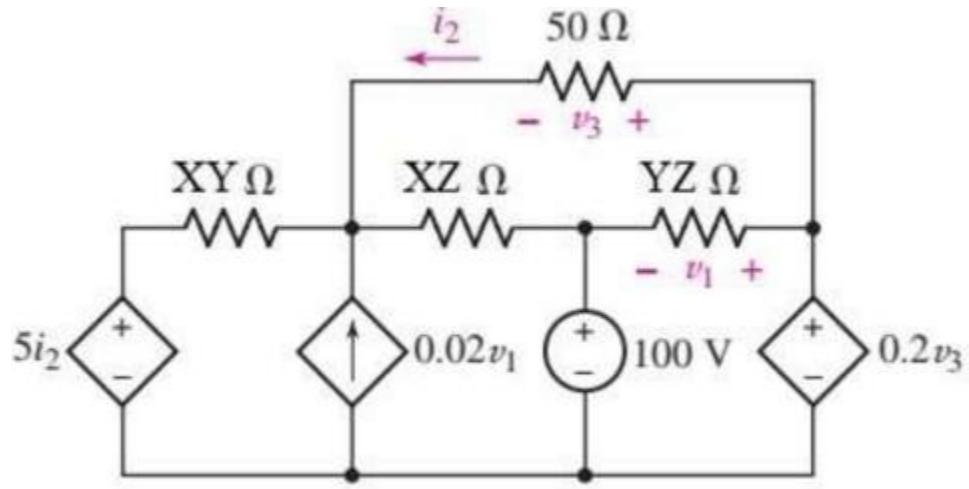


My ID : 1200549

X=5.

Y=4.

Z=9.

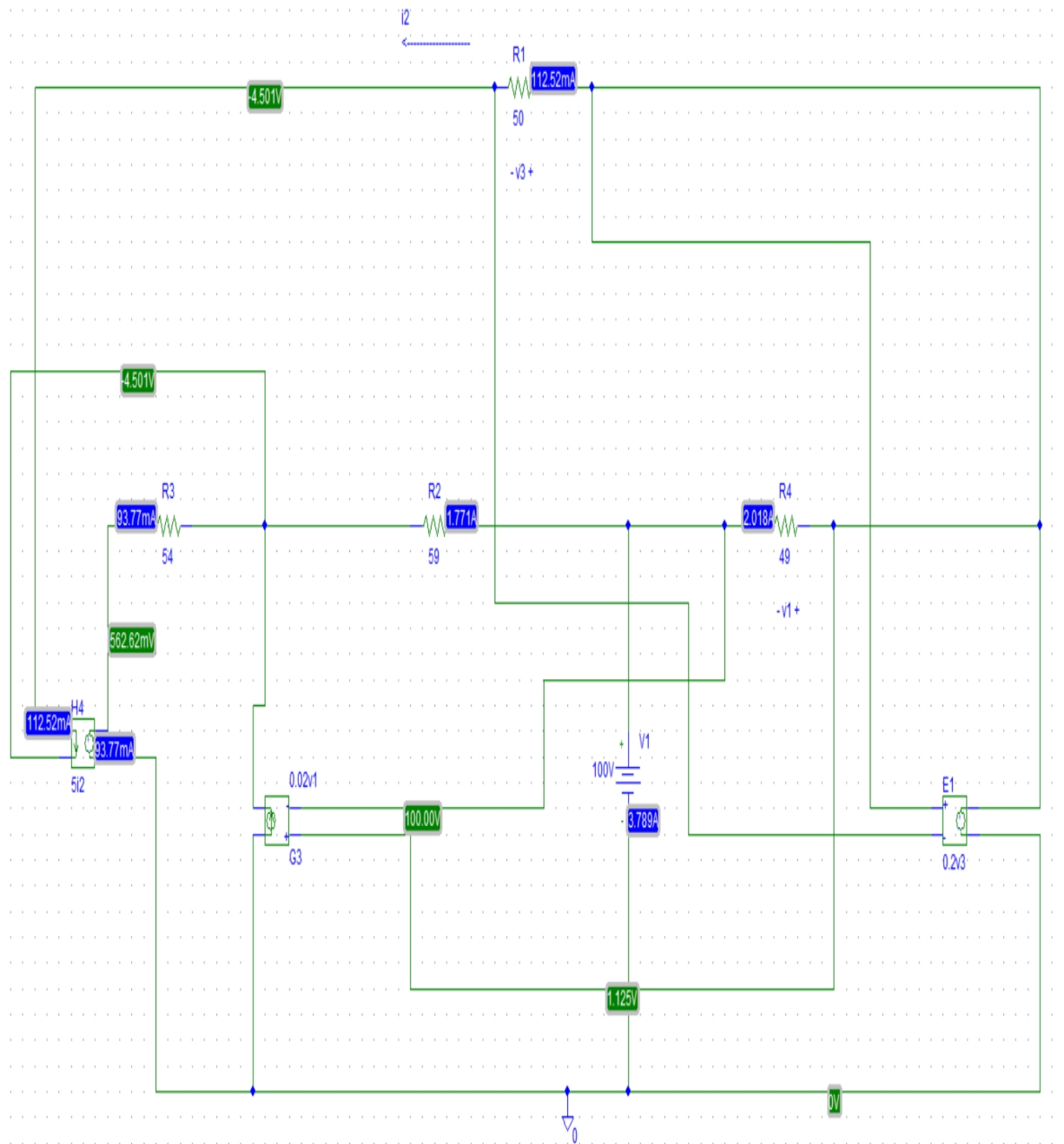

In this circuit, I use PSpice to implement this circuit, I used a dependent voltage source (E1) in this circuit, with a value equal 0.2 v3. In addition, I used a current source with voltage controlled (G3) with a value 0.02 v1, also I used a voltage source with current controlled (H4) with a value 5 i2. When I finished build the circuit, I press on simulate then run this circuit, and the values for voltages and currents appeared in the circuit below.


Question 2: The circuit shown in Figure below has two inputs, $v_s(t)$ and $i_s(t)$, and one output, $v(t)$. When inputs are given by $V_s(t) = V_m \sin 6t$ V and $i_s(t) = I_m$ A the output will be $v_o(t) = A \sin(6t + \theta) + B$ V. Linearity requires that A be proportional to V_m and that B be proportional to I_m . Consequently, we can write $A = k_1 V_m$ and $B = k_2 I_m$, where k_1 and k_2 are constants yet to be determined.

(a) Use PSpice to determine the value of k_1 by simulating the circuit, using $V_m = 1$ V and $I_m = 0$.

(b) Use PSpice to determine the value of k_2 by simulating the circuit, using $V_m = 0$ V and $I_m = 1$.

(c) Knowing k_1 and k_2 , specify the values of V_m and I_m that are required to cause $v_o(t) = 5 \sin(6t + \theta) + 5$ V. Simulate the circuit, using PSpice to verify the specified values of V_m and I_m .

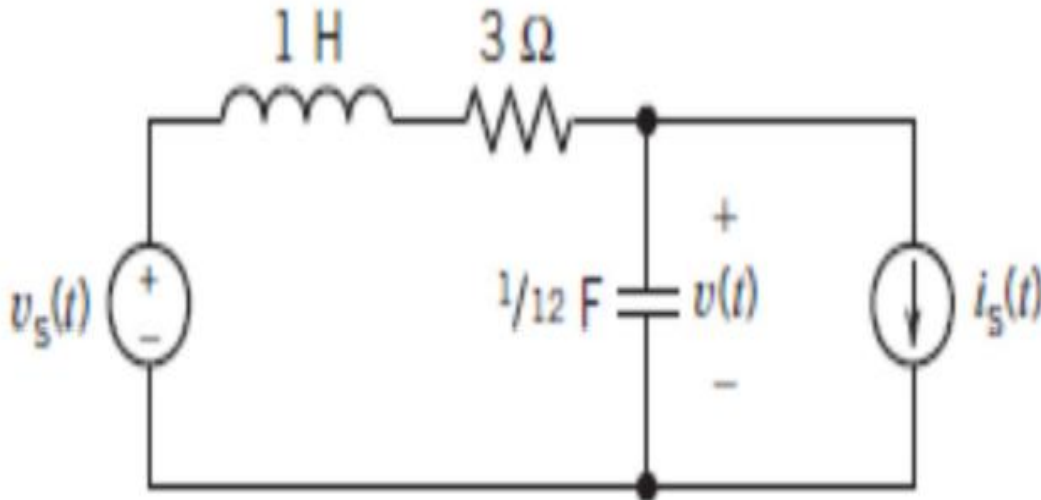(d) Determine the average power delivered by $v_s(t)$ using Pspice.




(a) Use PSpice to determine the value of k_1 by simulating the circuit, using $V_m = 1\text{ V}$ and $I_m = 0$.


When $V_m = 1\text{ V}$, and $I_m = 0\text{ A}$

$I_s(t) = 0\text{ A}$,, and $V_s(t) = \sin(6t)\text{ V}$, so $\omega = 6\text{ rad/s}$.. and the frequency equal $\omega/(2\pi) = 6/(2 \cdot 3.14) = 0.955\text{ Hz}$

I built the circuit below

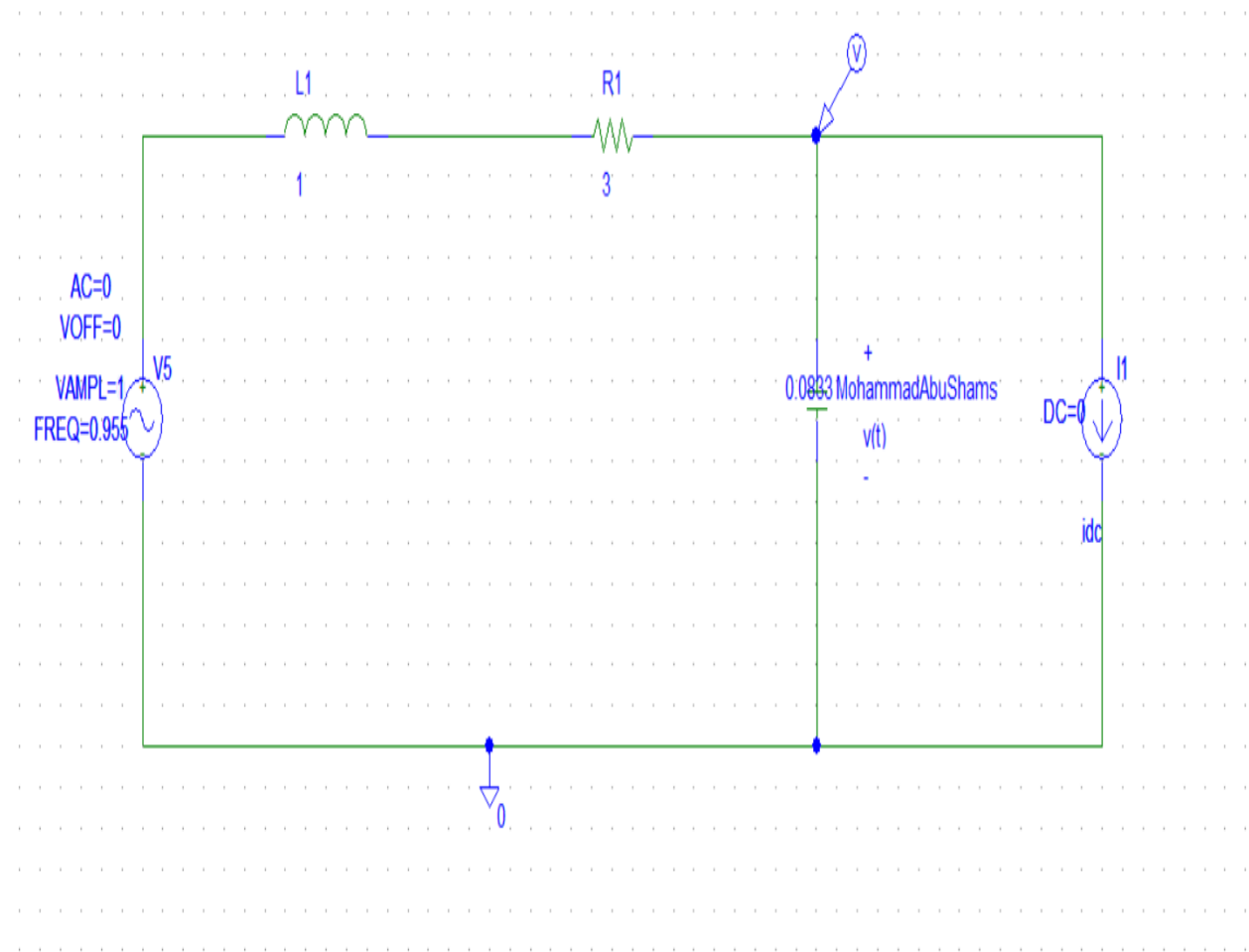

Waves:

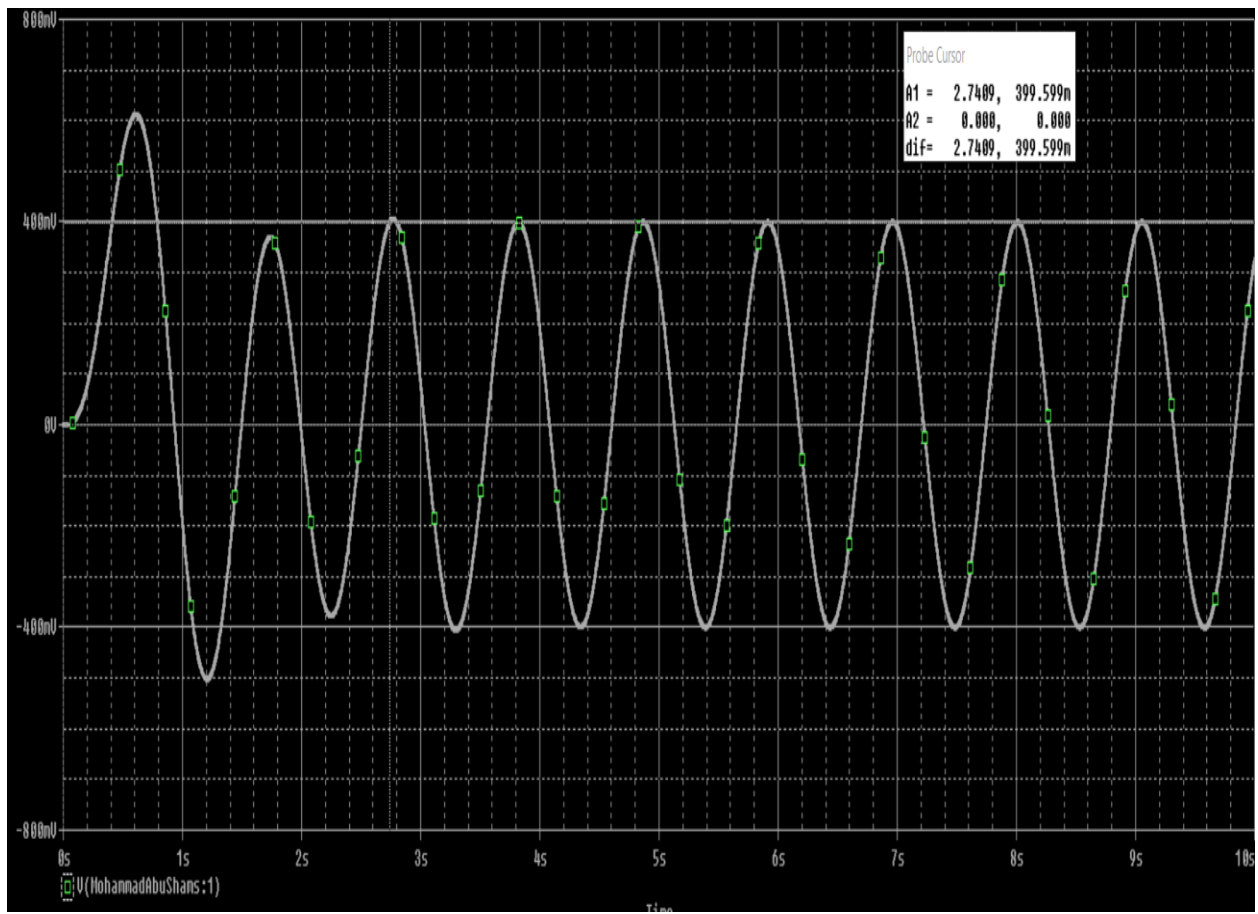

According to this diagram

the value of $K_1 = 399.599\text{m} / 1$

$= 0.4$

$k_1=0.4$

(b) Use PSpice to determine the value of k_2 by simulating the circuit, using $V_m = 0$ V and $I_m = 1$.


When $V_m = 0$ V, and $I_m = 1$ A

$I_s(t) = 1$ A ,, and $V_s(t) = 0$ V $\omega = 6$ rad/s .. and the frequency equal $\omega/(2\pi)$


$= 6/(2 \cdot 3.14) = 0.955$ Hz

And $A = k_1$,, $B = 0$.

I built the circuit below

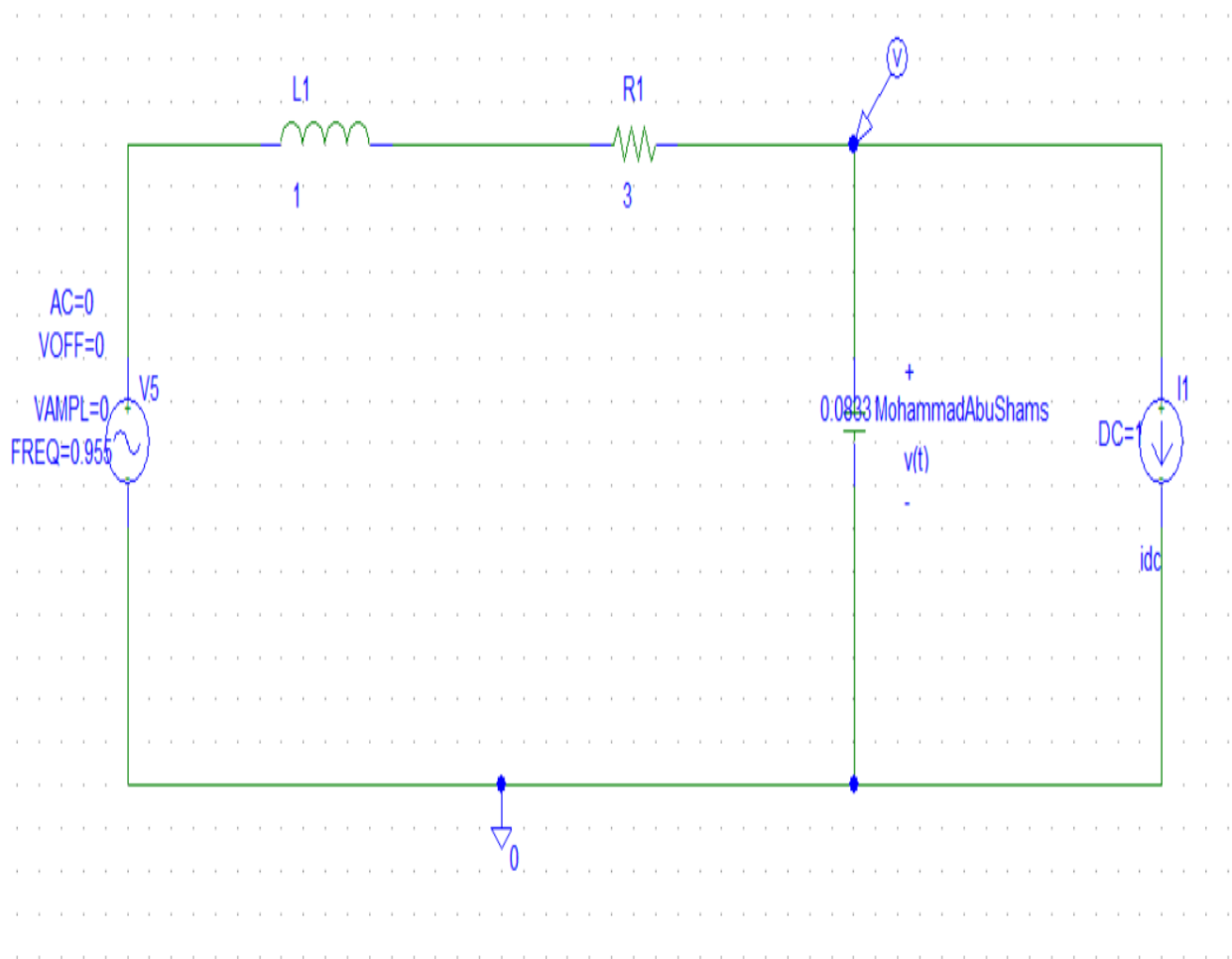

Waves:

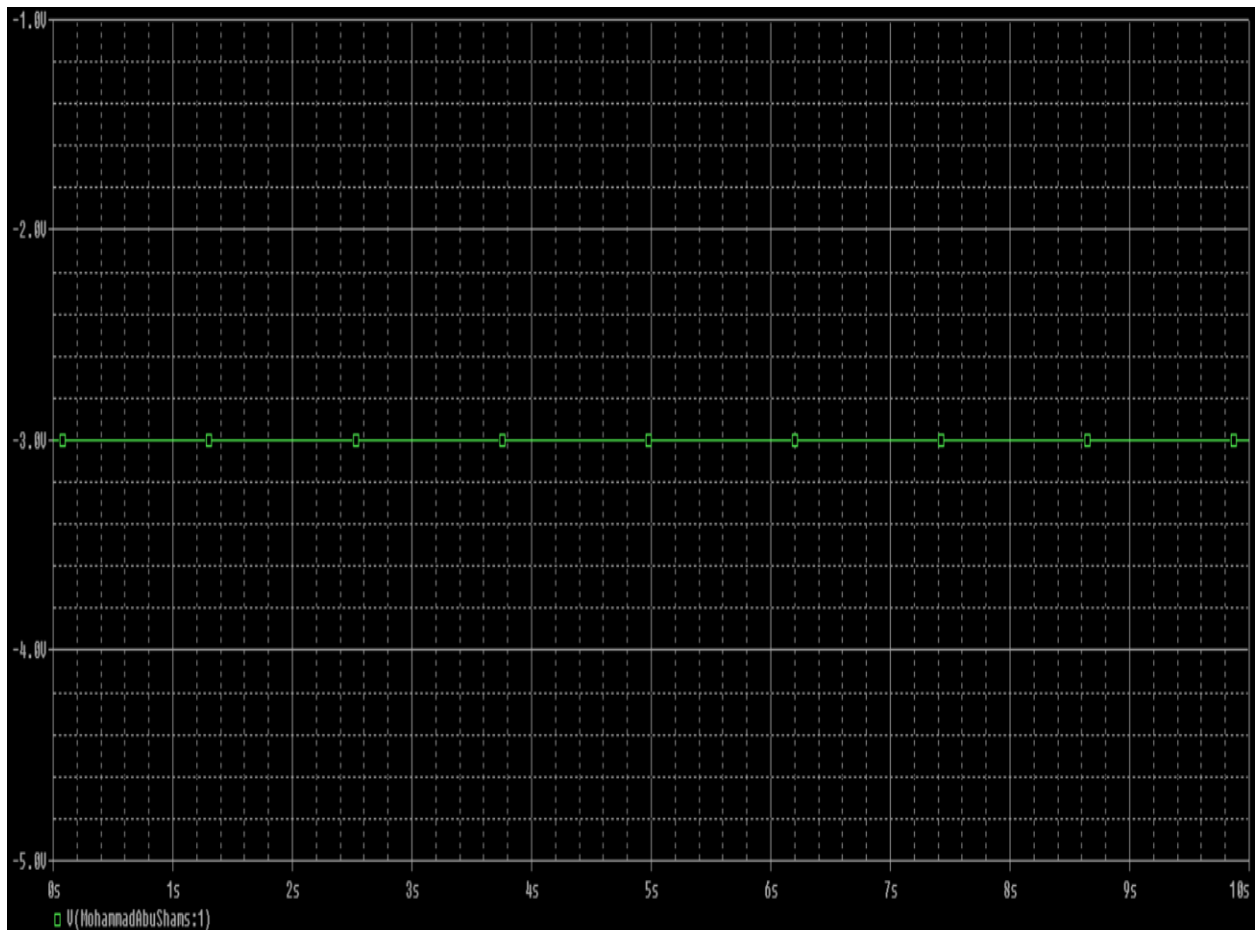

According to this diagram, the value of $K_2 = -3$

$k_2 = -3$

(c) Knowing k_1 and k_2 , specify the values of V_m and I_m that are required to cause $v_o(t)=5\sin(6t+\theta)+5$ V. Simulate the circuit, using PSpice to verify the specified values of V_m and I_m .

$$v_o(t)=5\sin(6t+\theta)+5 \text{ V}$$

For the voltage

1 input volt \rightarrow 0.4 output volt (k_1)

X input volt \rightarrow 5 output volt

$$\text{So, } X = (5 \cdot 1) / 0.4 = 5 / 0.4 = 12.5 \text{ volt}$$


For the current

1 input Ampere \rightarrow -3 output Ampere


X input Ampere \rightarrow 5 output Ampere

$$\text{So, } X = (5 \cdot 1) / -3 = 5 / -3 = -1.67 \text{ Ampere}$$

Then I built the circuit below

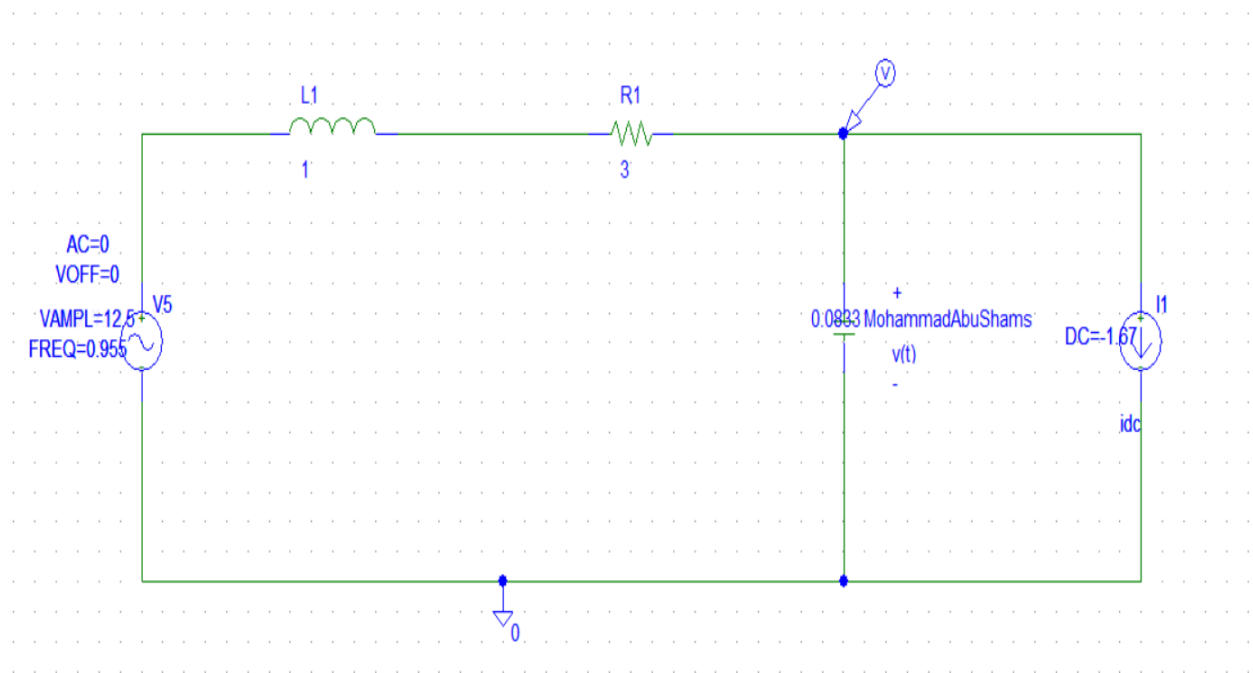


Waves:

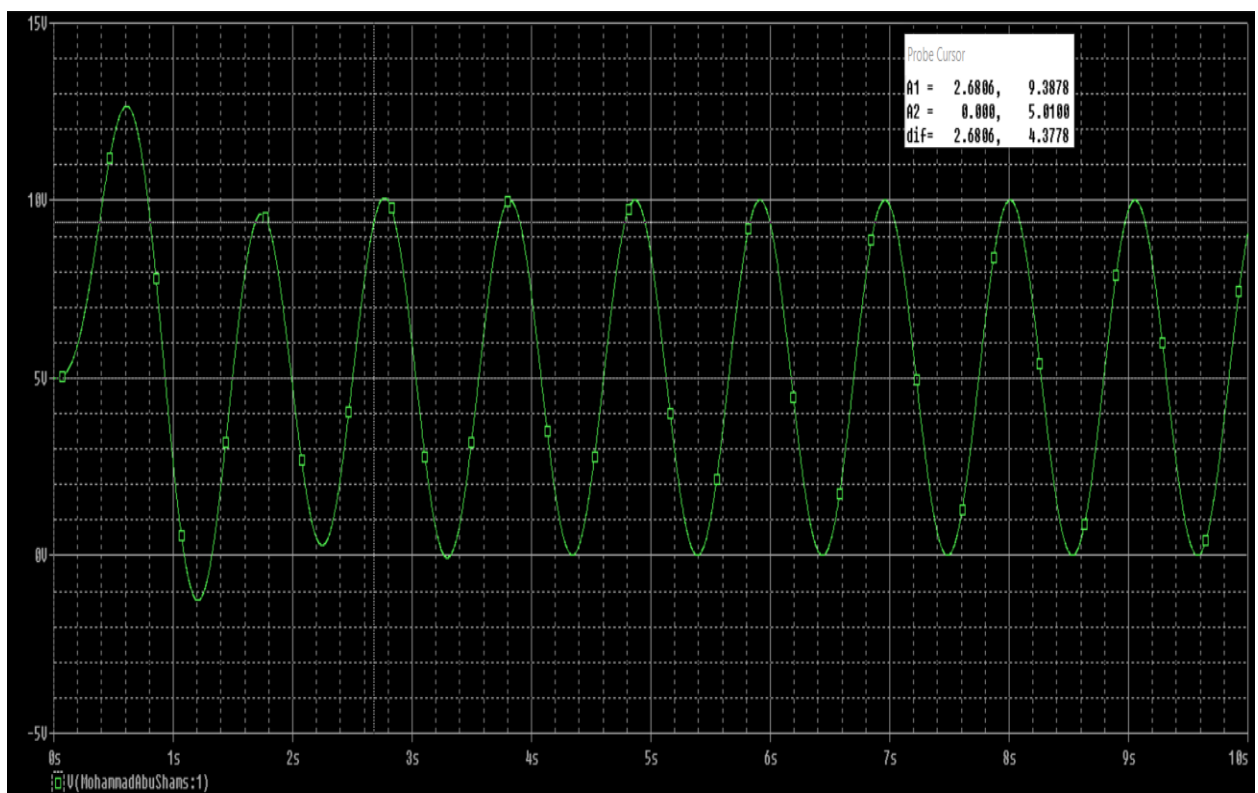

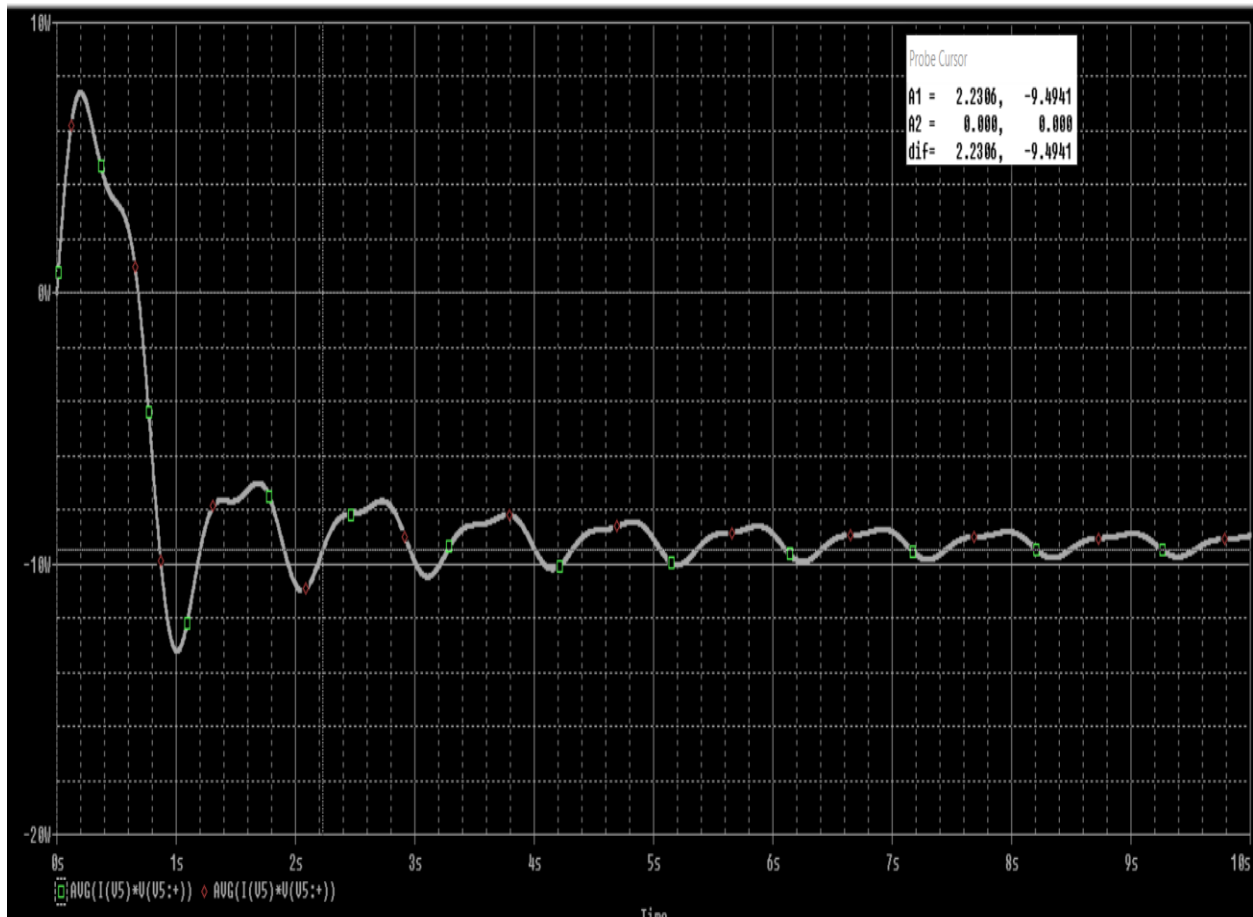(d) Determine the average power delivered by $v_s(t)$ using Pspice.

For the circuit before, After simulation, I pressed to the (trace) and then pressed to (add trace) then I added the voltage and the current



from this red diagram, I noticed that the average power = 9.5 watt delivered = -9.5 watt.

Approximately 10 watt.

Thank you Dr. Hakam Shehadeh